| ISN | | | | | |
|-----|-----|---|--|-----|--|
| | 0.0 | 7 | | 6 6 | |

18CS33

Analog and Digital Electronics

Time: 3 hrs. Max. Marks: 100

Third Semester B.E. Degree Examination, Dec.2019/Jan.2020

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- Explain the construction, working and characteristics of photo diode. (06 Marks) 1
 - With hysteresis characteristics explain the working of Schmitt trigger circuit (Inverting).

(06 Marks)

With a neat circuit diagram and mathematical analysis explain voltage divider bias circuit. (08 Marks)

- OR a. Explain the working of R-2R ladder D to A converter. (06 Marks)
 - b. Explain successive approximation A to D converter. (06 Marks)
 - Show how IC-555 timer can be used as an astable multivibrator. (08 Marks)

Module-2

- Find the minimum SOP and minimum POS expressions for the following function using K-map. $f(A, B, C, D) = \sum_{m} (1, 3, 4, 11) + \sum_{d} (2, 7, 8, 12, 14, 15)$. (06 Marks)
 - b. What are the disadvantages of K-map method? How they are overcome in Quine Mccluskey method. Simplify following function using Q-M method

 $f(A, B, C, D) = \sum_{m} (0, 1, 2, 5, 6, 7, 8, 9, 10, 14).$ (08 Marks) c. What is Map-Entered Variable method? Using MEV method simplify following function:

 $f(A, B, C, D) = \sum_{m} (2, 3, 4, 5, 13, 15) + dc(8, 9, 10, 11).$ (06 Marks)

- With the help of flow chart explain how to determine minimum sum of products using Karnaugh map. (06 Marks)
 - b. Using Q-M method simplify the following function

 $F(A, B, C, D) = \sum_{m}(2, 3, 7, 9, 11, 13) + \sum_{d}(1, 10, 15).$

(08 Marks)

With example explain Petrik's method.

(06 Marks)

Module-3

- 5 What are hazards in digital circuits? Explain different types of hazards. (06 Marks)
 - Implement full subtractor using 3 to 8 decoder and NAND gates.

(06 Marks)

Differentiate between PAL and PLA. Realize following functions using PLA. Give PLA table and internal connection diagram for the PLA (Use as many common terms as possible) $F_1(1, b, c, d) = \sum_{m} (1, 2, 4, 5, 6, 8, 10, 12, 14)$

 $F_2(a, b, c, d) = \sum_{m} (2, 4, 6, 8, 10, 11, 12, 14, 15)$

(08 Marks)

What is Multiplexer? Implement following function using 8:1 MUX

 $(A, B, C, D) = \sum_{m} (1, 2, 5, 6, 9, 12)$

(08 Marks)

- b. Design Hexadecimal (Binary) to ASCII Code Converter using suitable ROM. Give the connection diagram of ROM. (06 Marks)
- c. Explain Simulation and testing of digital circuits.

(06 Marks)

1 of 2

www.vturesource.com

ALL BRANCHES | ALL SEMESTERS | NOTES | QUESTON PAPERS | LAB MANUALS

A Vturesource Go Green initiative